

## Experiment-4

### **Aim:**

To implement a common gate amplifier of gain 10 and analyze its transient and ac characteristics.

### **Tool Used:**

LTspice

### **Theory:**

The common-gate (CG) amplifier for MOSFET is the analogue of the common base amplifier for BJT. Its popularity arises from its lower noise and ease of impedance matching.

For a Level 3 NMOS let's assume

$$V_{GS} = 0.6V$$


$$V_T = 0.4V$$

$$V_{DD} = 1.8V$$

$$K_n = 120\mu A/V^2,$$

Which gives a value of  $(W/L) = 416$  for  $1mA$   $I_D$ . Also, for these values'  $g_m$  is attained as  $10m\Omega^{-1}$ , therefore for gain 10,  $R_D$  is taken as  $1K\Omega$ . The value of  $V_{DS}$  should be maintained above  $(V_{GS} - V_T = 0.6 - 0.4 = 0.2V)$  for the transistor to stay in saturation region. As  $W/L$  is 416, the width is taken as  $416\mu m$  and the length is taken as  $1\mu m$ .

### **Circuit Schematic:**

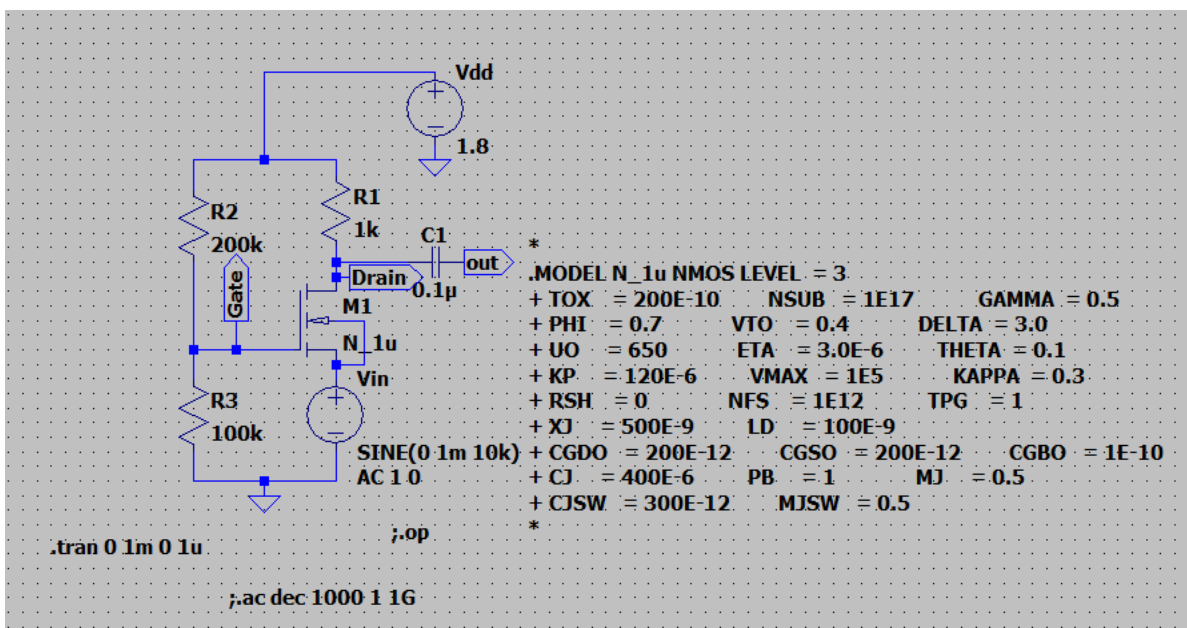

# Output Waveforms:


## DC operating Point

\* C:\Users\singh\Documents\Analog IC Design Lab\Lab4\commor


--- Operating Point ---

V(drain) :	0.299922	voltage
V(gate) :	0.6	voltage
V(n002) :	0	voltage
V(n001) :	1.8	voltage
V(out) :	2.99922e-008	voltage
Id(M1) :	0.00150011	device_current
Ig(M1) :	0	device_current
Ib(M1) :	-3.09921e-013	device_current
Is(M1) :	-0.00150011	device_current
I(C1) :	-2.99922e-020	device_current
I(R3) :	6e-006	device_current
I(R2) :	6e-006	device_current
I(R1) :	0.00150008	device_current
I(Vdd) :	-0.00150608	device_current
I(Vin) :	0.00150008	device_current

## Transient characteristics

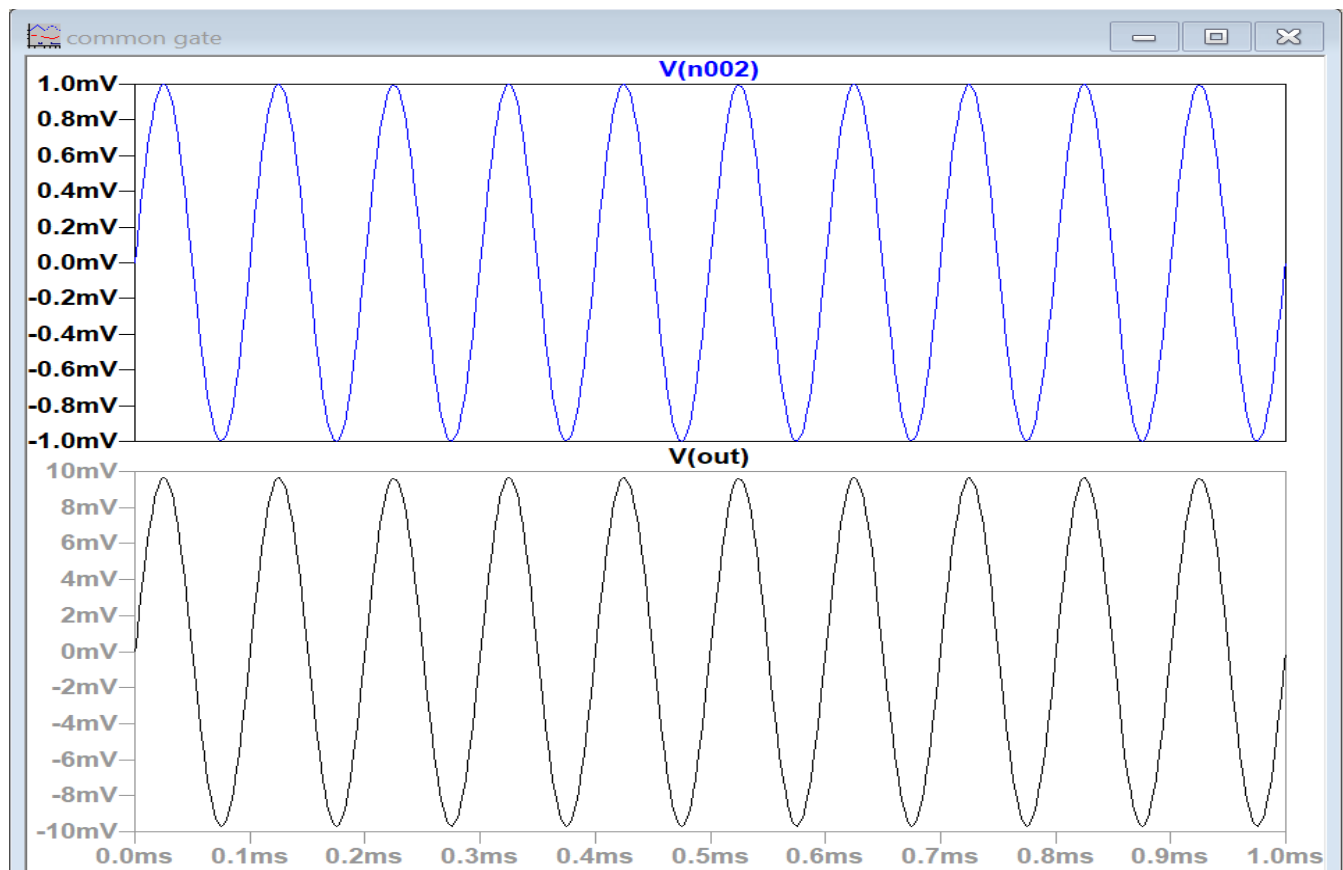

# AC Analysis

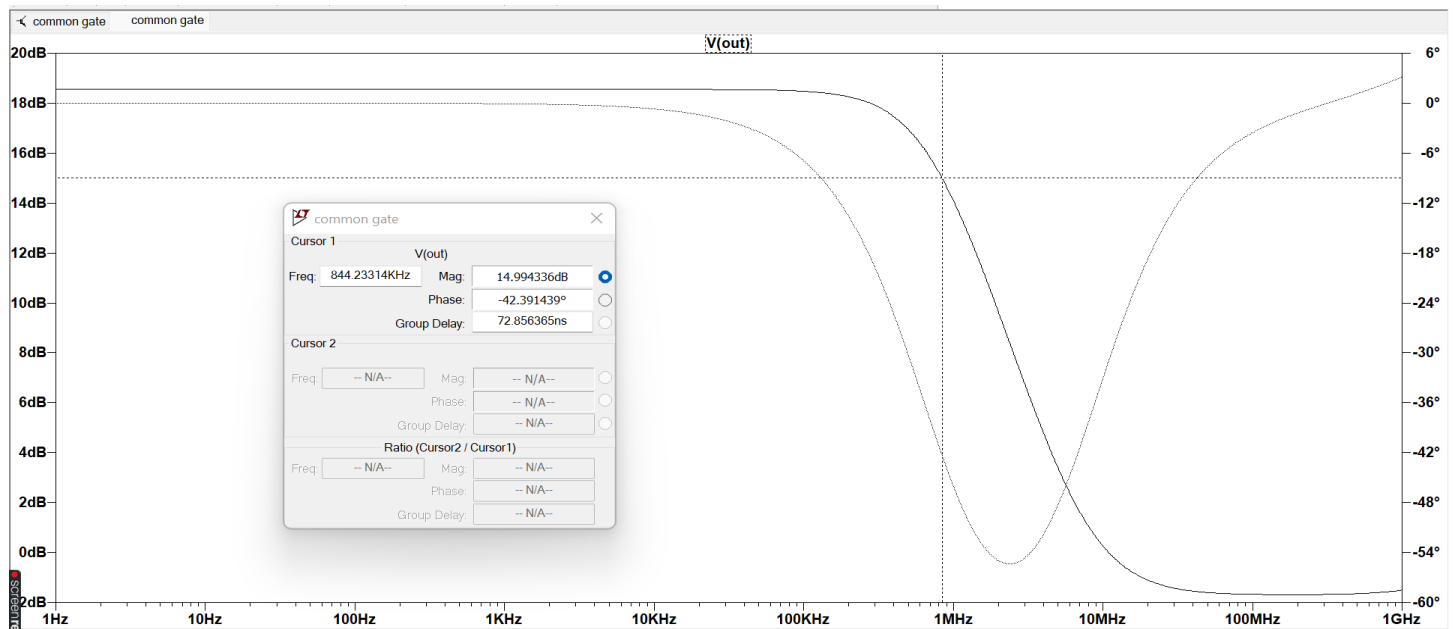

## Result:

The circuit is designed for a gain of 10 and the output is verified to be correct. The transient and AC characteristics are visualized.

Bandwidth,  $F_C = 844\text{KHz}$ .