

Experiment-2(B)

Aim:

To implement a Resistive Load inverter and analyze its transient and dc characteristics.


Tool Used:

LTspice

Theory:


The basic structure of a resistive load inverter is shown in the figure given below. Here, enhancement type nMOS acts as the driver transistor. The load consists of a simple linear resistor R_L . The power supply of the circuit is V_{DD} and the drain current I_D is equal to the load current I_R . When the input of the driver transistor is less than threshold voltage V_{TH} ($V_{in} < V_{TH}$), driver transistor is in the cut – off region and does not conduct any current. So, the voltage drop across the load resistor is ZERO and output voltage is equal to the V_{DD} . Now, when the input voltage increases further, driver transistor will start conducting the non-zero current and nMOS goes in saturation region.

Circuit Schematic:

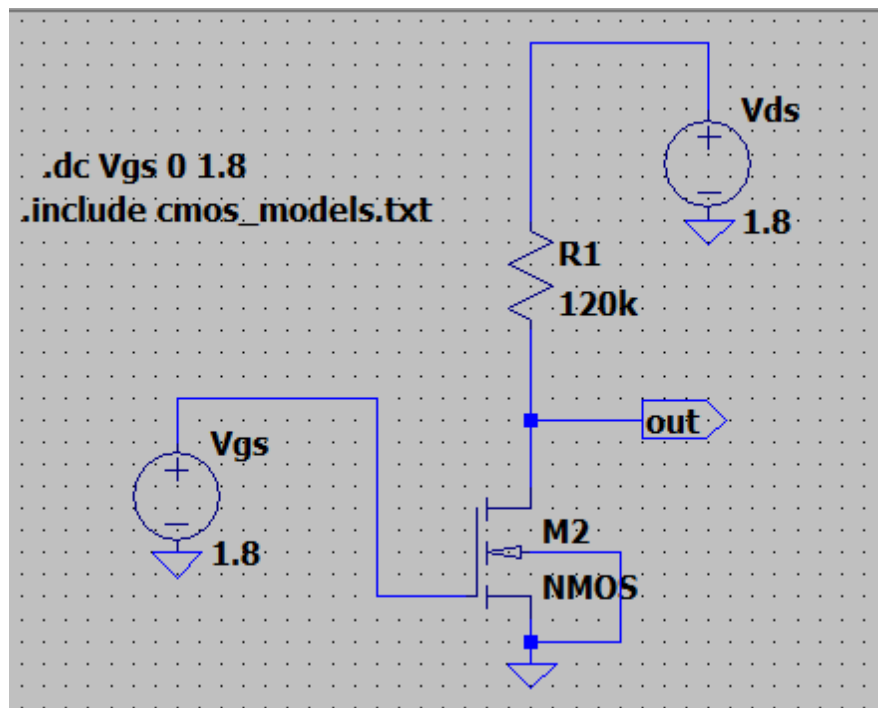


Output Waveforms:

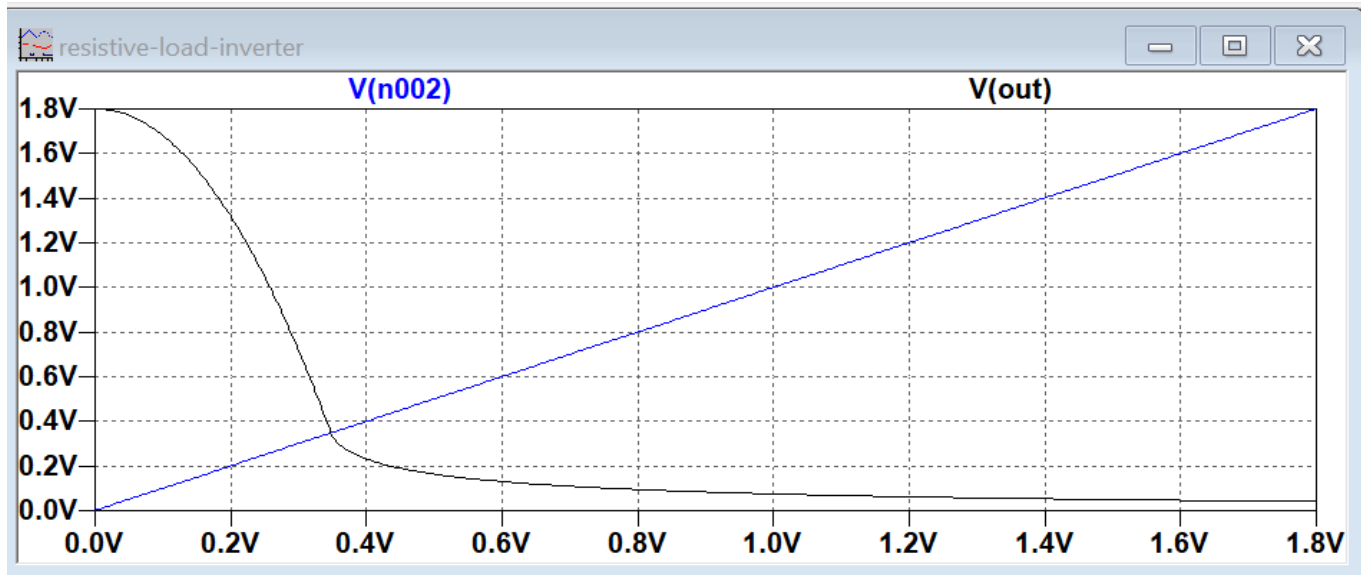Dc Transfer characteristics (V_{gs} vs. V_{out})



Transient characteristics

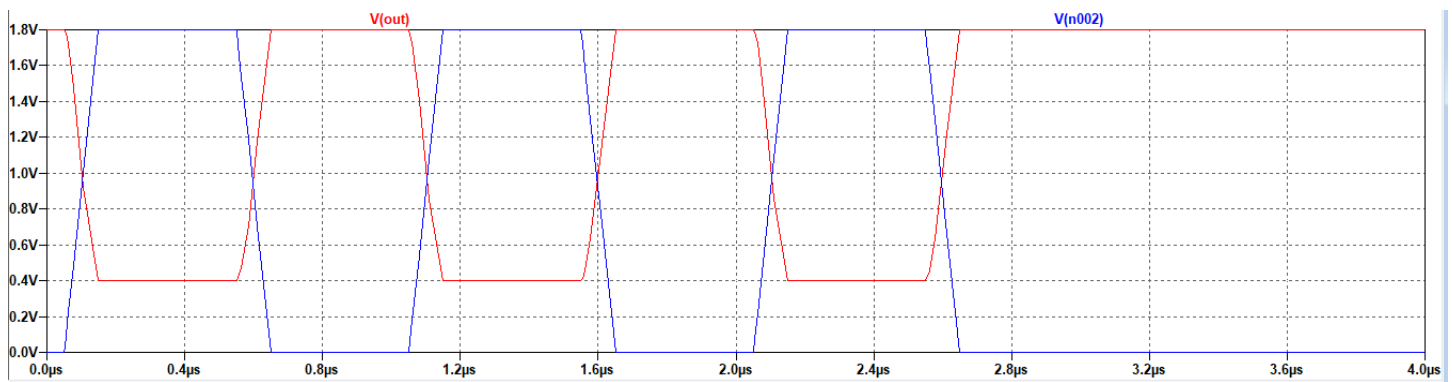

Result:

The circuit is stimulated with 120k resistor and the dc characteristics are visualized.