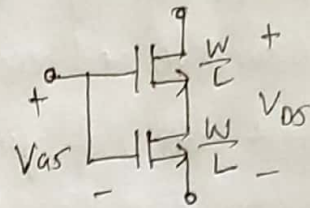


Assignment-1

① Based on Problem 2.16 of the Razavi's book:

Consider the structure shown in the following figure. Determine I_D as a function of V_{GS} and V_{DS} and prove that the structure can be viewed as a single transistor having an aspect ratio $W/(2L)$. Assume $\lambda = \gamma = 0$



case-1 M_1 : Triode, M_2 : Triode

$$V_{DD1} = V_{GS} - V_{th},$$

$$V_{DD2} = V_{GS} - V_x - V_{th}$$

$$V_{DS1} = V_x, \quad V_{DS2} = V_{DS} - V_x$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{th})V_x - V_x^2] \quad \text{--- ①}$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{th} - V_x)(V_{DS} - V_x) - (V_{DS} - V_x)^2]$$

$$I_{D1} = I_{D2}$$

$$2(V_{GS} - V_{th})V_x - V_x^2 = 2(V_{GS} - V_{th})V_{DS} + 2V_x^2 - 2V_x(V_{GS} - V_{th}) - 2(V_{DS} - V_x)^2 - V_{DS}^2 - V_x^2 + 2V_x V_{DS}$$

$$= 2[2(V_{GS} - V_{th})V_x - V_x^2] = 2(V_{GS} - V_{th})V_{DS} - V_{DS}^2 \quad \text{--- ②}$$

from eq ① & ②

$$I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \times \frac{1}{2} [2(V_{GS} - V_{th})V_{DS} - V_{DS}^2] \Rightarrow \frac{W}{2L} \text{ is in triode}$$

case-2 M_1 : Triode, M_2 : saturation

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{th})V_x - V_x^2] \quad \text{--- ③}$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_x - V_{th})^2$$

$$I_{D1} = I_{D2}$$

$$V_x^2 - 2V_x(V_{GS} - V_{th}) + (V_{GS} - V_{th})^2 = 2(V_{GS} - V_{th})V_x - V_x^2$$

$$(V_{GS} - V_{th})^2 = 2[2(V_{GS} - V_{th})V_x - V_x^2] \quad \text{--- ④}$$

from eq ③ & ④

$$I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \times \frac{1}{2} (V_{GS} - V_{th})^2 \Rightarrow \frac{W}{2L} \text{ is in saturation}$$

$$\text{as } V_{GS} - V_{th} \geq 0 \Rightarrow V_{GS} - V_x - V_{th} > 0 \Rightarrow V_{GS} - V_{th} > V_x$$

$$V_{GS1} - V_{th} > V_{DS1} \Rightarrow M_1 \text{ is in triode}$$

It means the equivalent transistor is in saturation, if M_2 is in saturation and vice versa.


- ② Repeat part ① of question for the following structure (assuming both transistors have the same aspect ratio W/L) and show that the structure can be viewed as a single transistor having an aspect ratio of $2W/L$.

At point A

$$I_{D1} + I_{D2} = I$$



$$\Rightarrow \frac{1}{2} \mu_n C_{ox} \frac{2W}{L} (V_{GS} - V_{th})^2$$

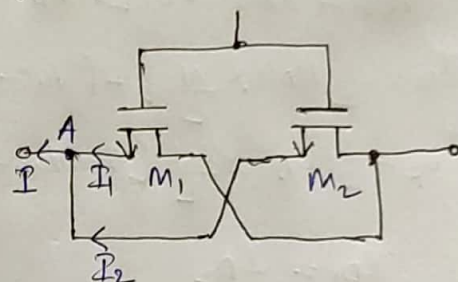\Rightarrow which equals the transistors to be a single transistor of $2W$ width.



- ③ Calculate the output resistance (V_x/I_x) of following circuit. Assume $\lambda \neq 0$ and $r \neq 0$

①

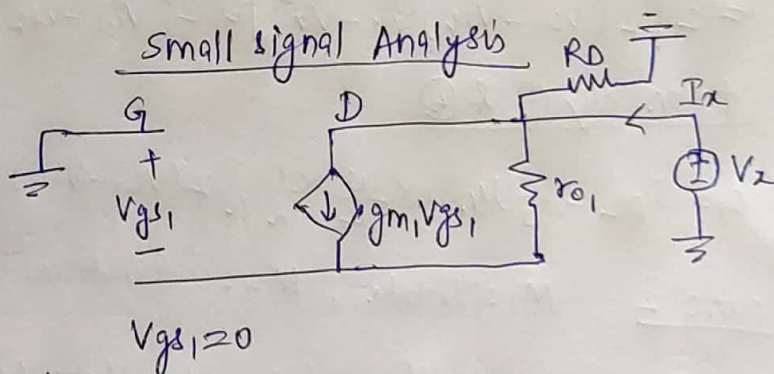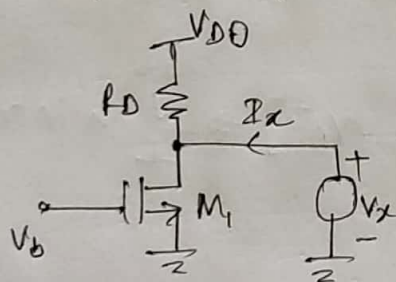


Applying KCL in output node.

$$I_x = \frac{V_x}{r_{o1}} + \frac{V_x}{R_D}$$


$$\boxed{\frac{V_x}{I_x} = \frac{r_{o1} R_D}{r_{o1} + R_D}}$$

$$\text{or } \boxed{\frac{V_x}{I_x} = r_{o1} \parallel R_D}$$

⑥

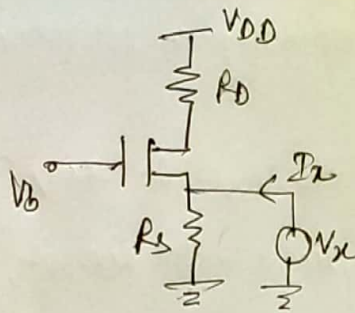

Small signal Analysis

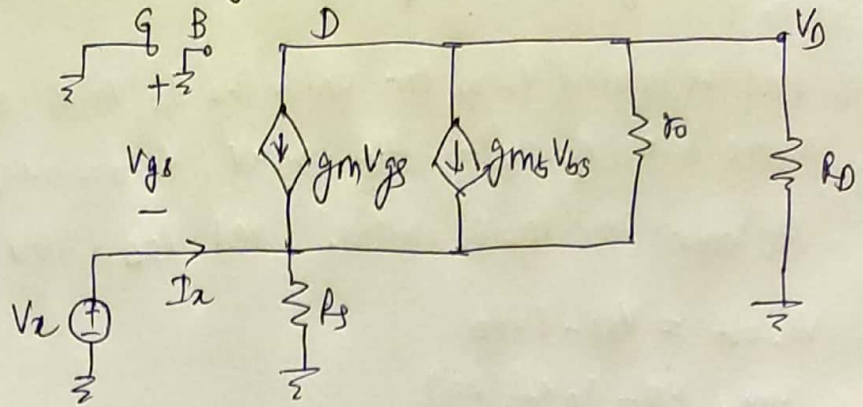

$$V_{gs} = -V_x$$

$$g_m V_{gs} = -g_m V_x$$

$$g_{mb} V_{bs} = g_{mb} (0 - V_x) = -g_{mb} V_x$$

Apply KCL at drain terminal:

$$\frac{V_D}{R_D} + \frac{V_D - V_x}{r_o} + g_m V_{gs} + g_{mb} V_{bs} = 0$$

$$\frac{V_D}{R_D} + \frac{V_D - V_x}{r_o} - g_m V_x - g_{mb} V_x = 0$$

$$V_D \left[\frac{1}{R_D} + \frac{1}{r_o} \right] = V_x \left[\frac{1}{r_o} + g_m + g_{mb} \right] \quad \text{--- ①}$$


Apply KCL at source terminal

$$I_x = \frac{V_x}{R_S} + \frac{V_D}{R_D} = \frac{V_x}{R_S} + \frac{1}{R_D} \left[\frac{\frac{1}{r_o} + g_m + g_{mb}}{\frac{1}{R_D} + \frac{1}{r_o}} \right] V_x$$


$$I_x = V_x \left[\frac{1}{R_S} + \frac{\frac{1}{r_o} + g_m + g_{mb}}{1 + \frac{R_D}{r_o}} \right]$$

$$\frac{V_x}{I_x} = \frac{R_S R_D + R_S r_o}{r_o + R_D + R_S + (g_m + g_{mb}) r_o R_S}$$

⑦

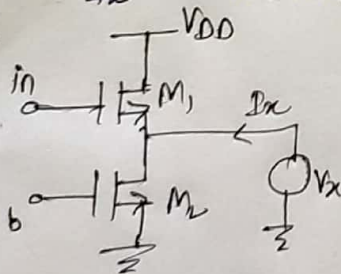

small signal analysis

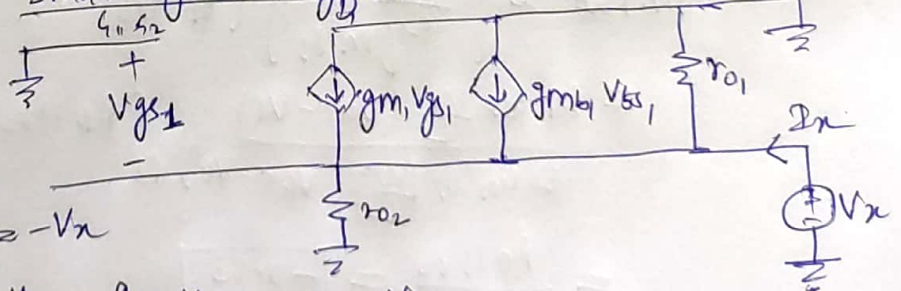

$$V_{gs1} = -V_x, \quad V_{bs1} = 0 - V_x = -V_x$$

KCL

$$I_x = \frac{V_x}{R_{D2}} + \frac{V_x}{r_{o1}} - g_{m1} V_{gs1} - g_{mb1} V_{bs1}$$

$$= \frac{V_x}{R_{D2}} + \frac{V_x}{r_{o1}} + g_{m1} V_x + g_{mb1} V_x$$

$$I_x = V_x \left[\frac{1}{R_{D2}} + \frac{1}{r_{o1}} + g_{m1} + g_{mb1} \right]$$

$$\boxed{\frac{V_x}{I_x} = \frac{1}{g_{m1} + g_{mb1} + \frac{1}{R_{D2}} + \frac{1}{r_{o1}}}}$$

① In the following ckt, assuming that the transistor is operating in saturation region:

② Find the required V_{bias} for which the dc value of the V_{out} is $1.44V$

Assume $\lambda = 0$, $\eta = 1V^{1/2}$, $2\phi_F = 0.64V$, $V_{th0} = 0.4V$, $\mu_n C_{ox} = 800 \mu A/V^2$,

$(\frac{W}{L})_{nmos} = 20$, $R_D = R_S = 20.5k\Omega$, and $V_{DD} = 1.8V$

$$V_{dc-out} = V_{dd} - I_D R_D$$

$$1.44 = 1.8 - I_D \times \left(\frac{1}{2} k\Omega\right)$$

$$I_D = (1.8 - 1.44) \text{ mA}$$

$$= 0.36 \times 2 = \boxed{0.72 \text{ mA}}$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

$$V_{th} = V_{th0} + r(\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F}) = 0.6V$$

$$V_{GS} = V_{bias} - I_D R_D = V_{bias} - 0.36$$

$$0.72 \times 10^{-3} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{bias} - 0.36 - V_{th})^2$$

$$\boxed{V_{bias} = 1.26V}$$

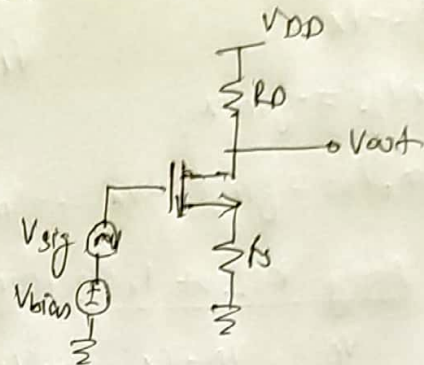

③ Is the assumption that the transistor is in saturation region?

$$V_{GS} = 1.26 - 1.44 < V_{th}$$

saturation

④ Find the small-signal gain V_{out}/V_{sig}

$$\text{As } G_{m \text{ out}} \approx \left(\frac{g_m}{1 + g_m R_S} \right) (R_D || R_o)$$

$$= \frac{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{th}) R_S} (R_D || R_o)$$

$$= \frac{R_D || R_o}{R_S} = \boxed{-0.53}$$