

Experiment -8

Aim:

1. Design an inverting and non-inverting amplifier using opamp using an F/B network
2. Determine bandwidth of amplifier using ac analysis
3. Evaluate the open-loop gain. Loop gain and close loop gain of both the amplifier (VFB/VTEST) and do ac analysis
4. Comment on the stability of the feedback amplifier

Apparatus used: LTSpice software


Theory:

An Operational Amplifier, or op-amp for short, is fundamentally a voltage amplifying device designed to be used with external feedback components such as resistors and capacitors between its output and input terminals

Op-amp Parameter and Idealised Characteristic


- Open Loop Gain, (A_{vo}): Infinite
- Input impedance, (Z_{IN}): Infinite
- Output impedance, (Z_{OUT}): Zero
- Bandwidth, (BW): Infinite
- Offset Voltage, (V_{IO}): Zero

Inverting amplifier:

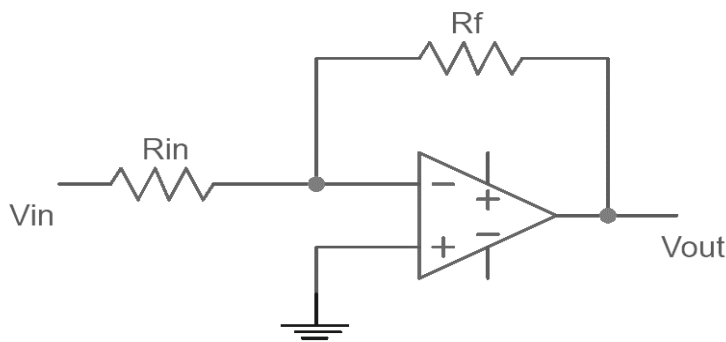


$$\text{Gain} = V_{out}/V_{in} = R_f/R_{in}$$

Non Inverting amplifier:

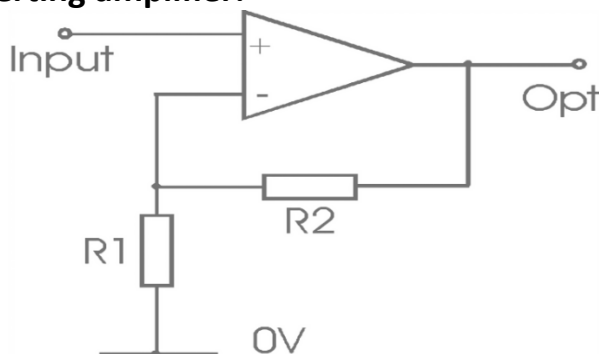

$$A_{CL} = \frac{V_{out}}{V_{in}} = \left(1 + \frac{R_1}{R_2}\right)$$

Circuit Schematic: INVERTING AMPLIFIER:

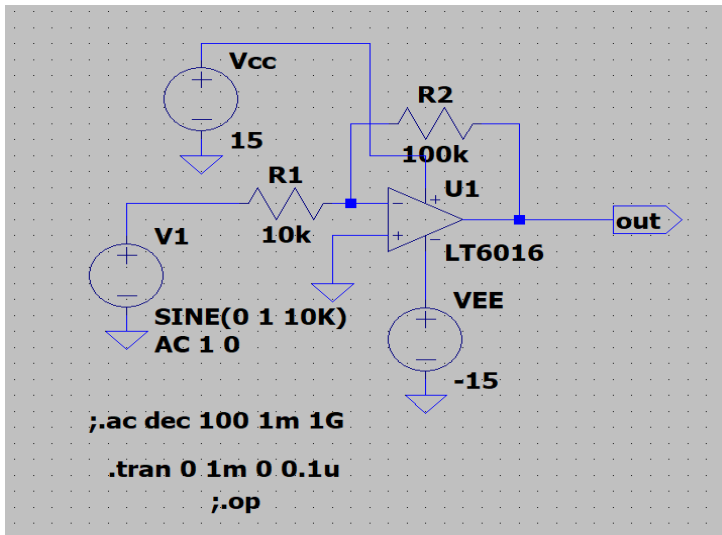


DC operating Point:

* C:\Users\singh\Documents\LTSpice\Analog IC Design Lab\Lab8\inv


--- Operating Point ---

V(n004) :	-15	voltage
V(n001) :	15	voltage
V(out) :	0.000176517	voltage
V(n002) :	-2.01981e-008	voltage
V(n003) :	0	voltage
I(R2) :	1.76537e-009	device_current
I(R1) :	-2.01981e-012	device_current
I(Vee) :	0.000345921	device_current
I(Vcc) :	-0.000345919	device_current
I(V1) :	-2.01981e-012	device_current
Ix(u1:1) :	1.76743e-009	subckt_current
Ix(u1:2) :	1.76739e-009	subckt_current
Ix(u1:3) :	0.000345919	subckt_current
Ix(u1:4) :	-0.000345921	subckt_current
Ix(u1:5) :	-1.75084e-009	subckt_current


Output Waveform: Transient response:

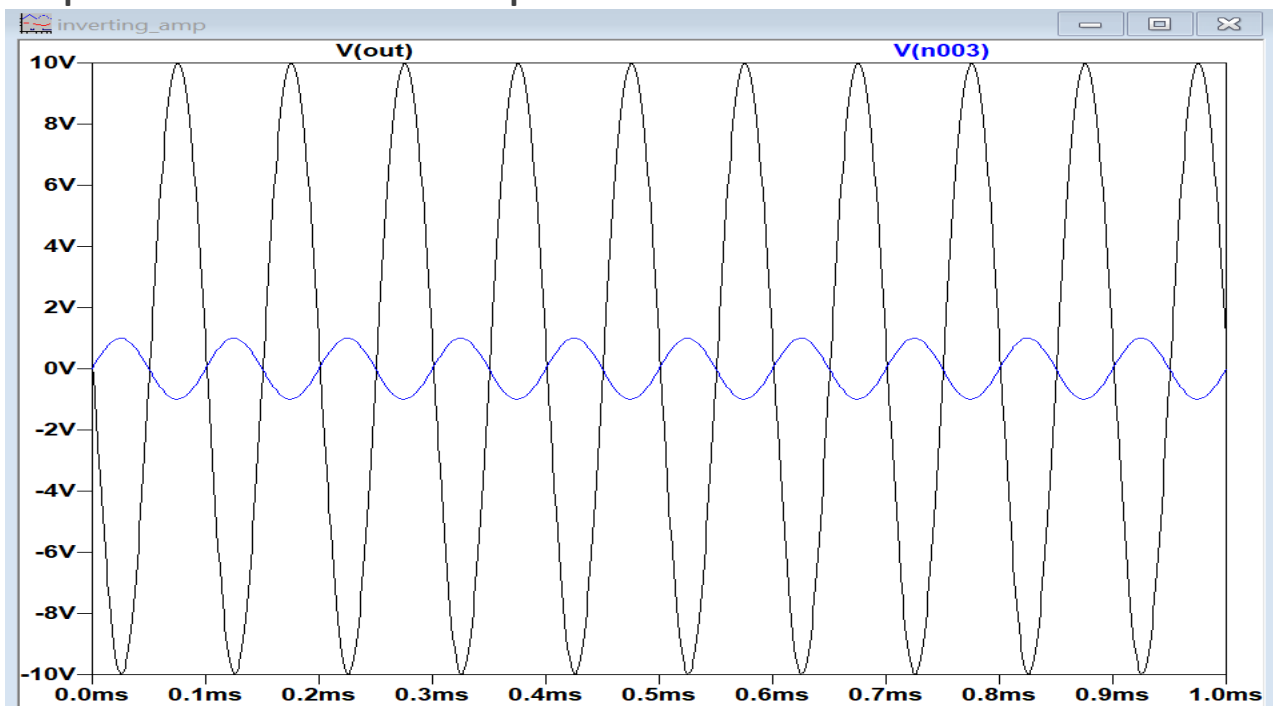


AC response:

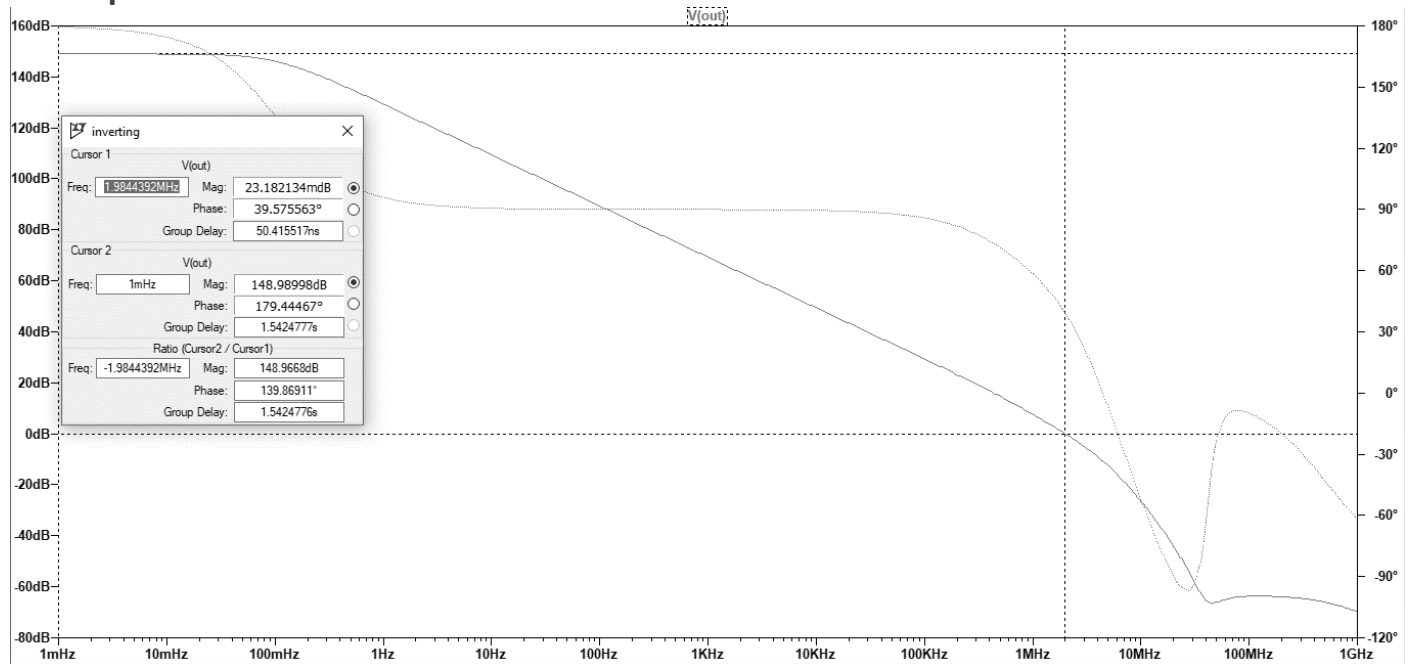


Inverting amplifier with VTest input

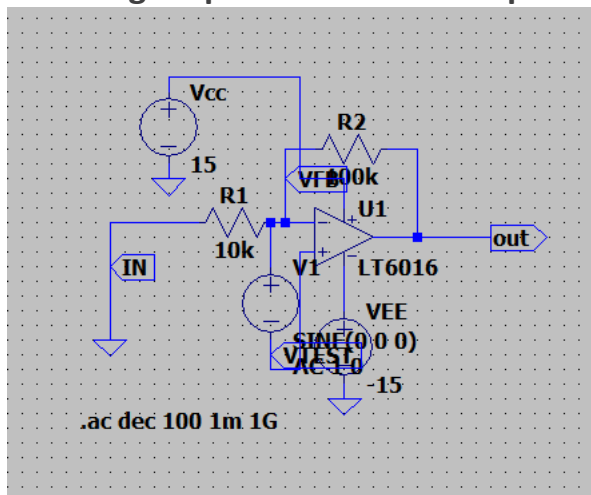

Waveform:

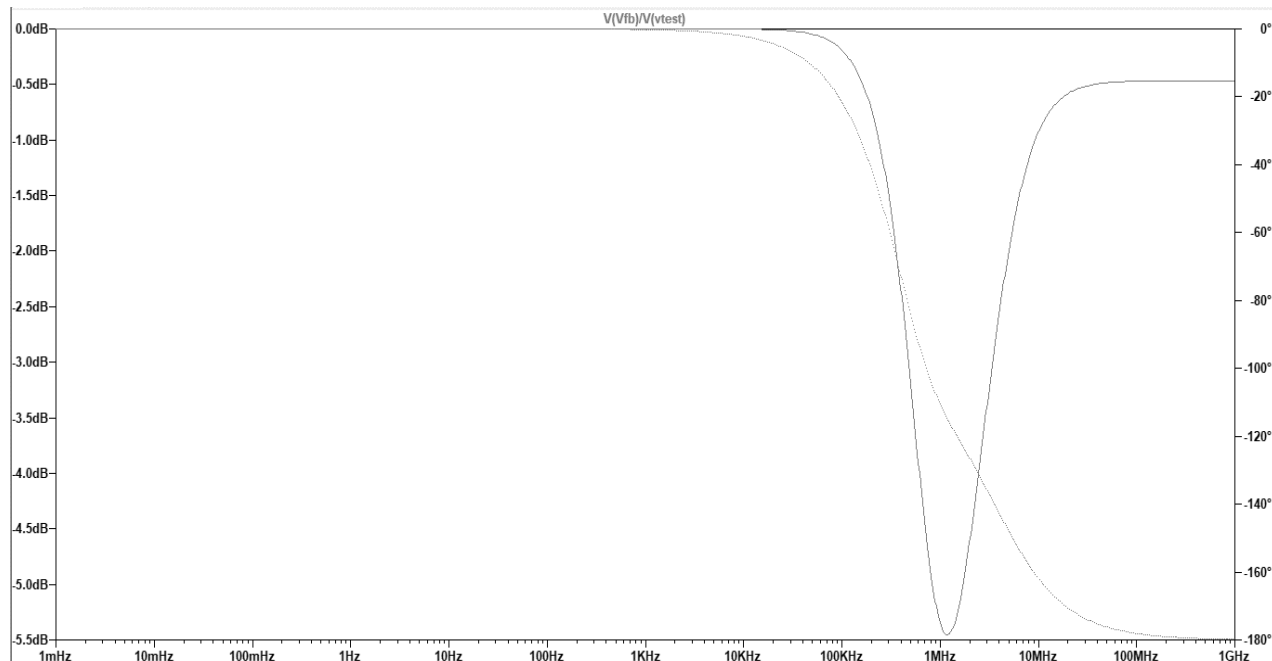

NON-INVERTING AMPLIFIER: Open-Loop

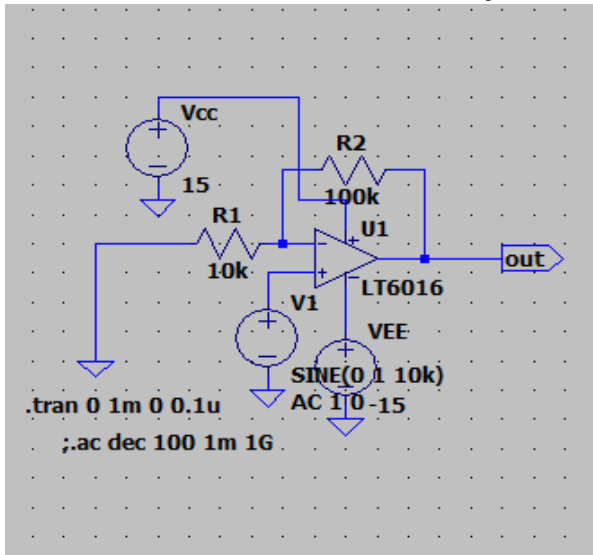


Operating point:


* C:\Users\singh\Documents\LTSpice\Analog IC Design Lab\Lab6

--- Operating Point ---


V(n004) :	-15	voltage
V(n001) :	15	voltage
V(out) :	0.000176517	voltage
V(n003) :	0	voltage
V(n002) :	-2.01981e-008	voltage
I(R2) :	1.76537e-009	device_current
I(R1) :	-2.01981e-012	device_current
I(V1) :	-1.76743e-009	device_current
I(Vee) :	0.000345921	device_current
I(Vcc) :	-0.000345919	device_current
Ix(u1:1) :	1.76743e-009	subckt_current
Ix(u1:2) :	1.76739e-009	subckt_current
Ix(u1:3) :	0.000345919	subckt_current
Ix(u1:4) :	-0.000345921	subckt_current
Ix(u1:5) :	-1.75084e-009	subckt_current

AC response:

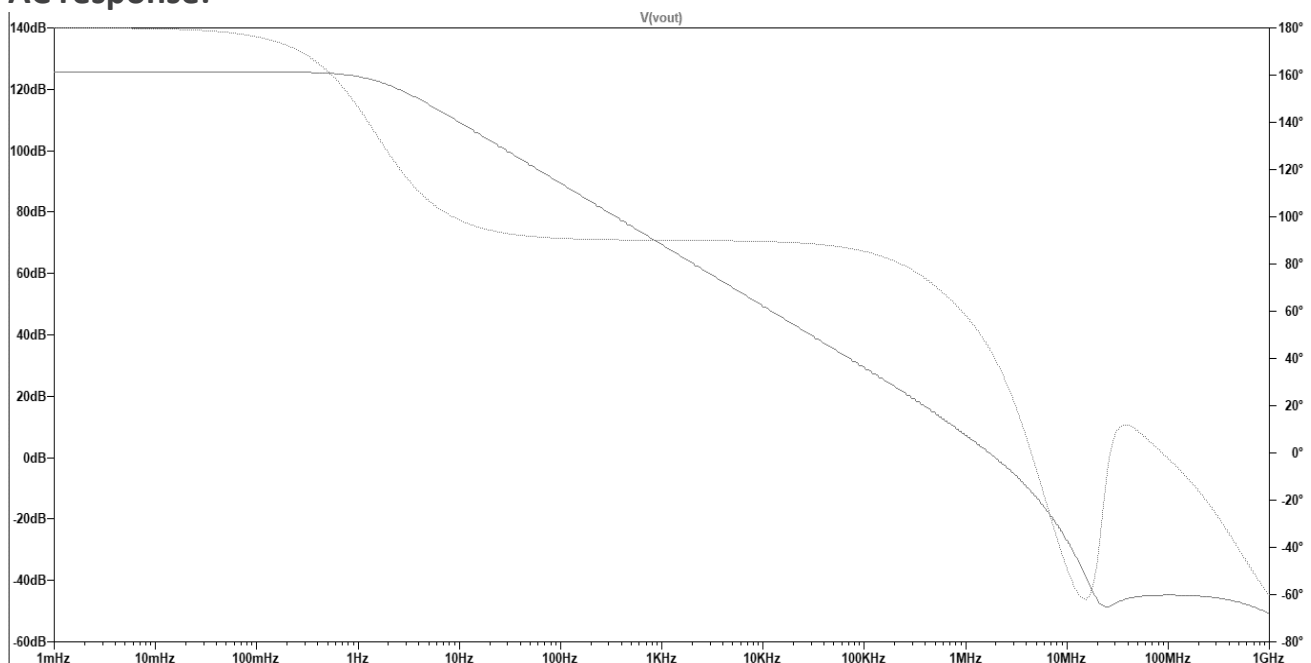


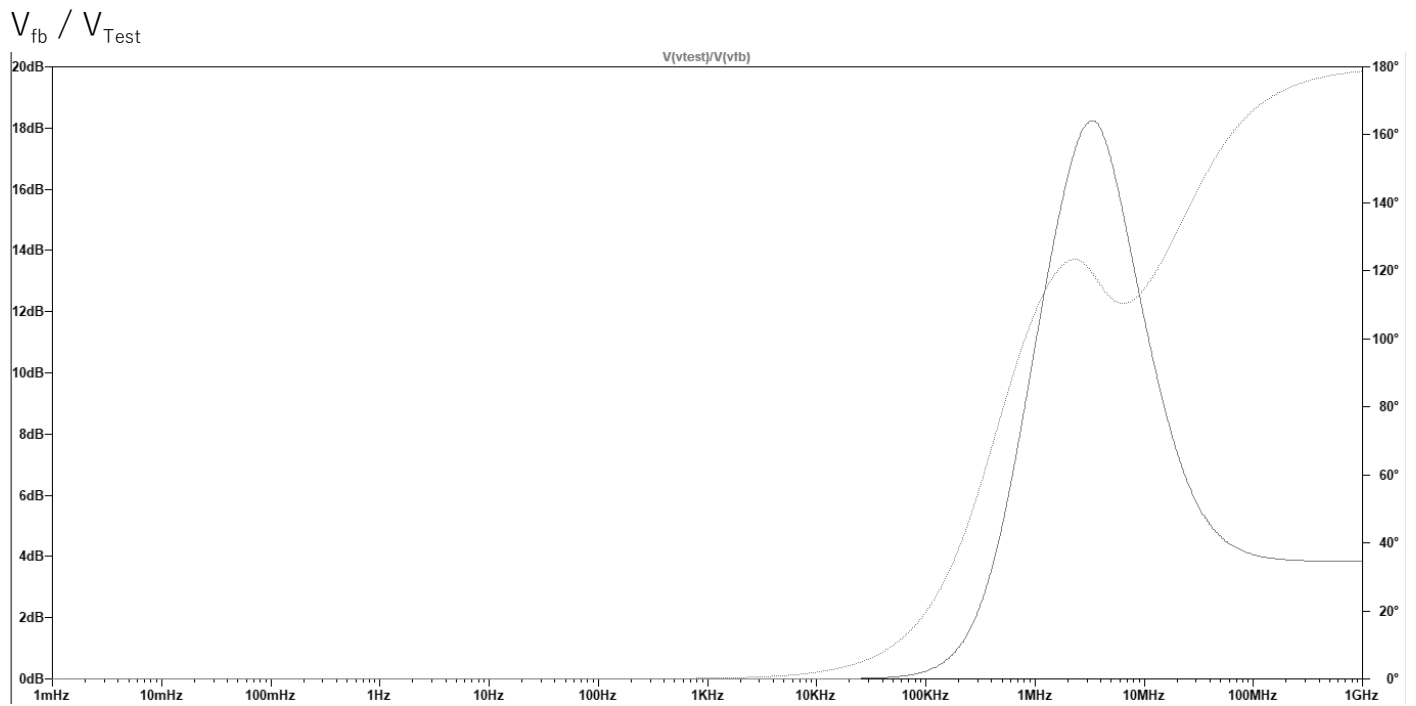


CLOSED-LOOP: CIRCUIT:

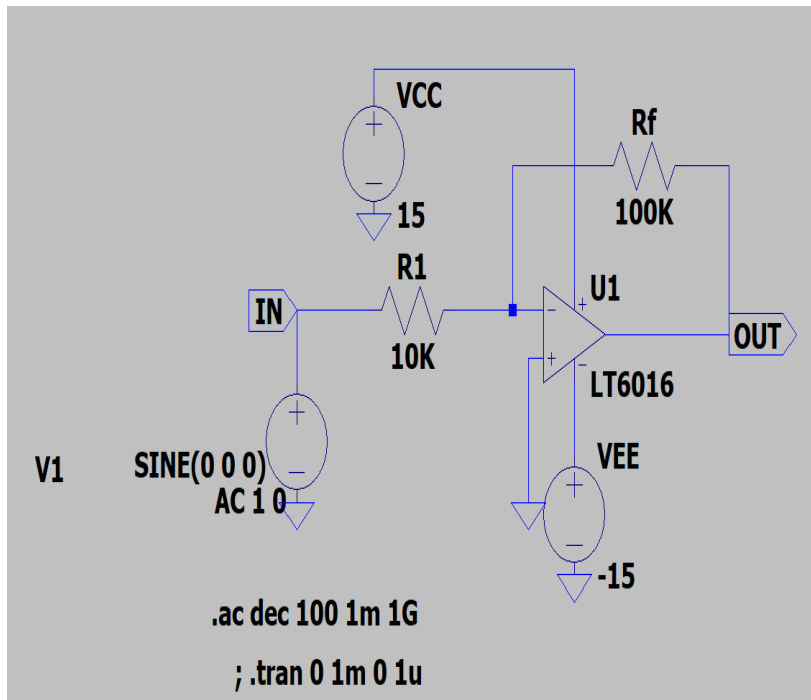

OUTPUT:

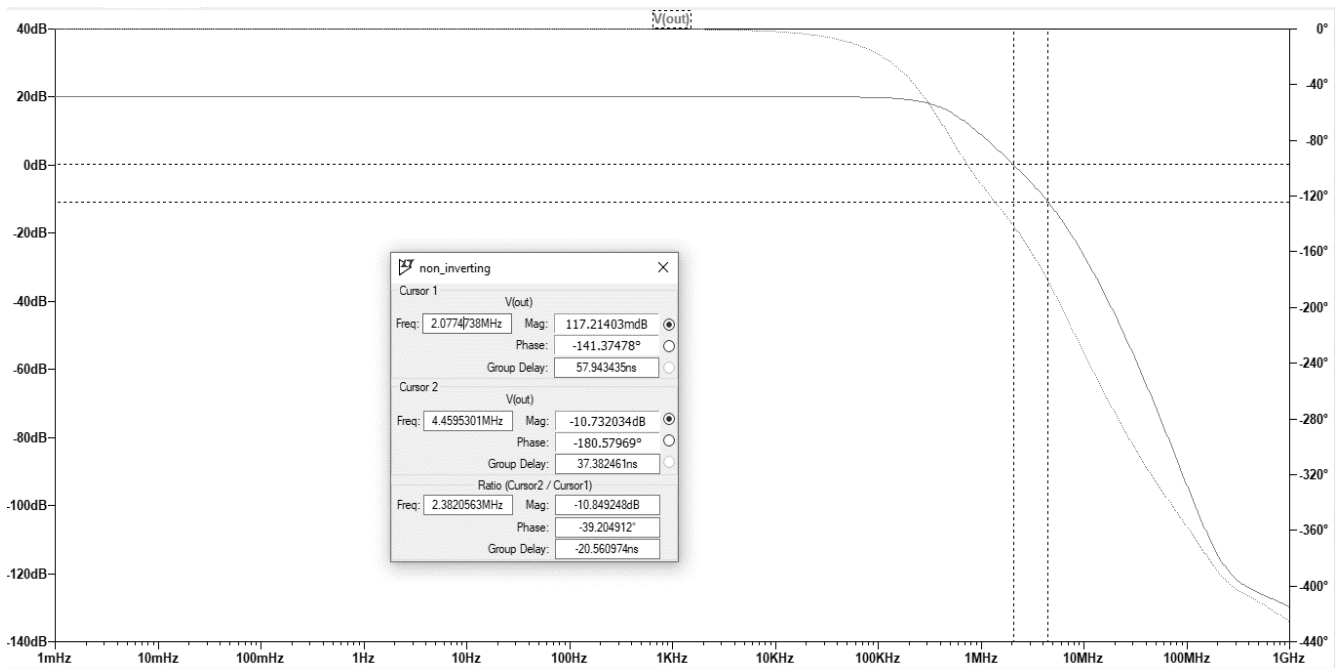

TRANSIENT:

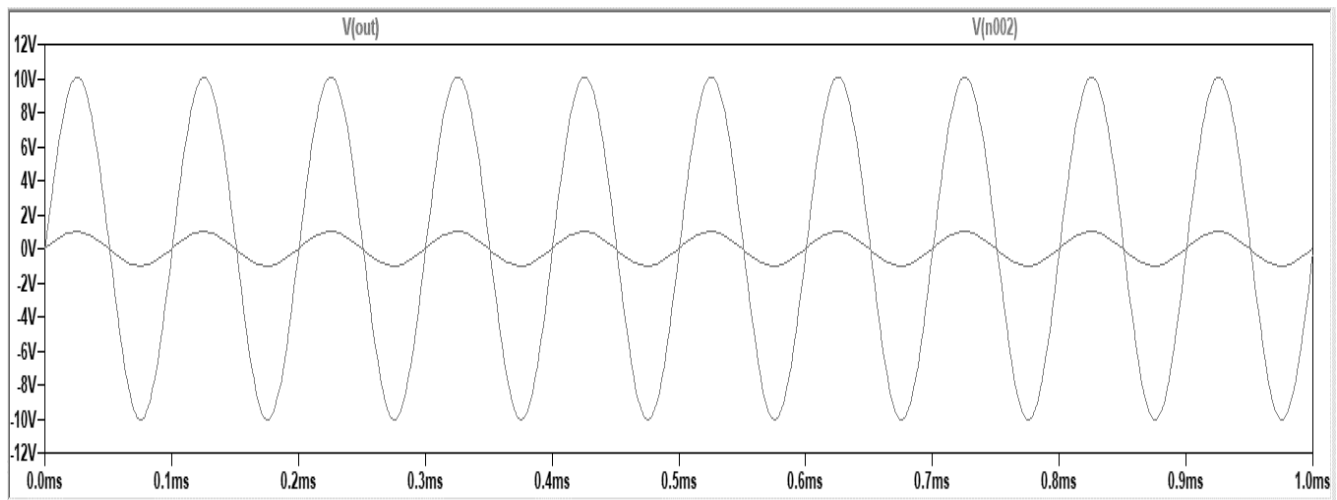

Observation:

Open-loop:

$W_{gc} = 1.984\text{MHz}$. The phase doesn't cross -180 degrees so the system is stable.

Closed loop:

$W_{gc} = 2.07\text{MHz}$, $W_{pc} = 4.45\text{MHz}$.

$W_{gc} < W_{pc}$, so the system is stable.

Phase Margin = -39.2 degrees

Gain Margin = 10dB

Closed loop gain = 10

Result:

The Experiment has been performed with both configurations of OpAmp and found to be correct.